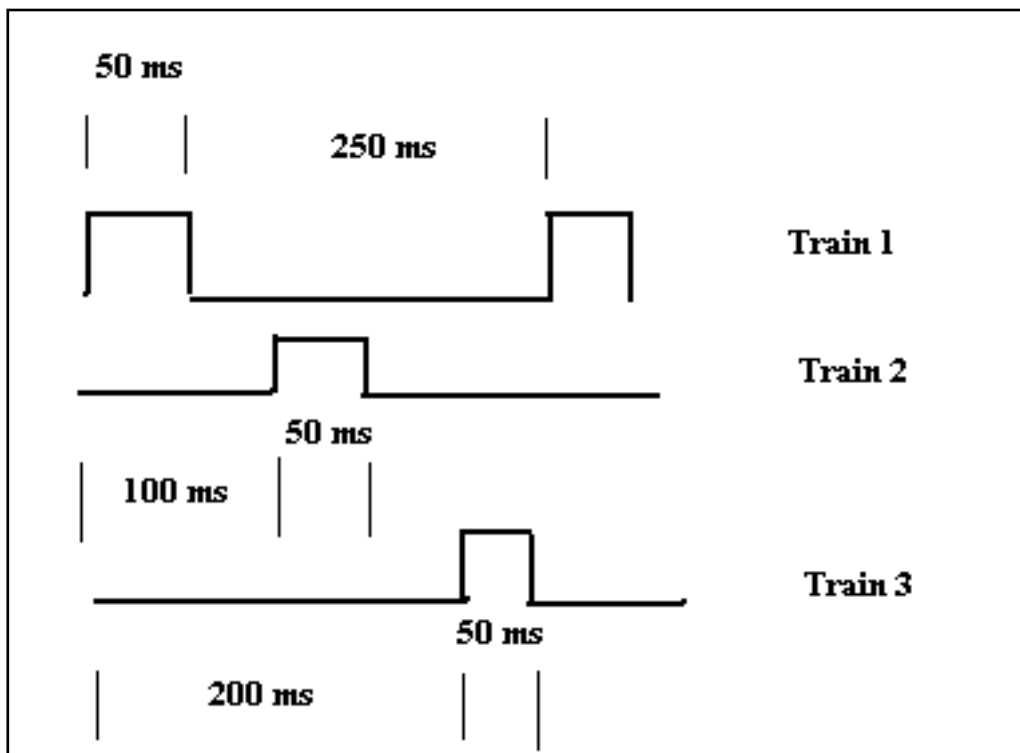


2.



Design:

An astable Multivibrator is used to produce a waveform with an on time on 250 microseconds and off time of 50 microseconds.

U1- Astable

Assume $C1=100\mu F$

$$T2=50 \text{ usec}=\ln(2)*Rb*C \quad Rb / R2=721.5k$$

$$T1=250 \text{ usec}=\ln(2)*(Ra+Rb)*C \quad Ra / R1=2.89k$$

The output of the astable multivibrator triggers a monostable multivibrator to produce a waveform with an on time on 50 microseconds and off time of 250 microseconds.

U2- Monostable (Generates Train 1)

Assume $C16=10 \mu F$

$$T=50 \text{ msec}=\ln(3)*Ra*C \quad Ra / R5=4.545k$$

The output of the monostable multivibrator triggers a monostable multivibrator to produce a waveform with an on time on 50 microseconds and off time of 250 microseconds.

U3 - Monostable

Assume $C6=10\mu F$

$$T=50 \text{ usec}=\ln(3)*Ra*C$$

$$Ra / R7=4.545k$$

The output of the monostable multivibrator triggers a monostable multivibrator to produce a waveform with an on time on 50 microseconds and off time of 250 microseconds.

U4 - Monostable (Generates Train 2)

Assume $C3=10\mu\text{F}$

$$T=50 \text{ usec}=\ln(3)*R_a*C$$

$$R_a / R3=4.545k$$

The output of the monostable multivibrator triggers a monostable multivibrator to produce a waveform with an on time on 50 microseconds and off time of 250 microseconds.

U5 - Monostable

Assume $C10=10\mu\text{F}$

$$T=250 \text{ usec}=\ln(3)*R_a*C$$

$$R_a / R6=4.545k$$

The output of the monostable multivibrator triggers a monostable multivibrator to produce a waveform with an on time on 50 microseconds and off time of 250 microseconds.

U6 - Monostable (Generates Train 3)

Assume $C13=10\mu\text{F}$


$$T=50 \text{ usec}=\ln(3)*R_a*C$$

$$R_a / R10=4.545k$$


Connecting C2 C4 C7 C5 C11 C14 all equals 10nF and connected to pin 5 of 555 timer to block DC.

Working:

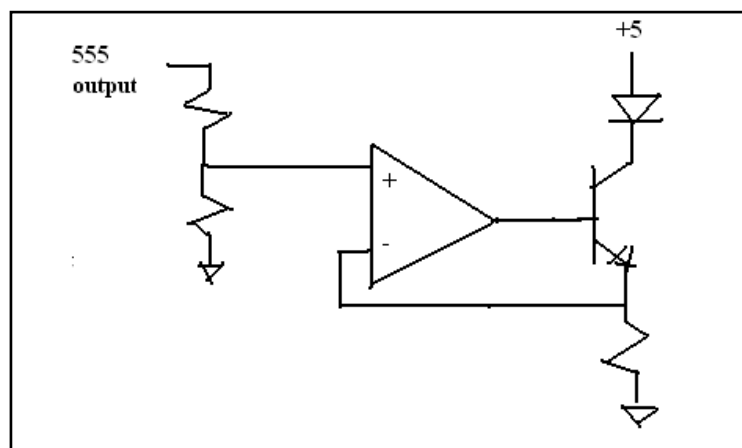
With the connection of 555 timers in series we are able to generate the three trains of impulse with an on duration of 50 milliseconds. With the following arrangement shown below we can generate constant current to drive the LED



LTSPICE SIMULATION- DESIGN

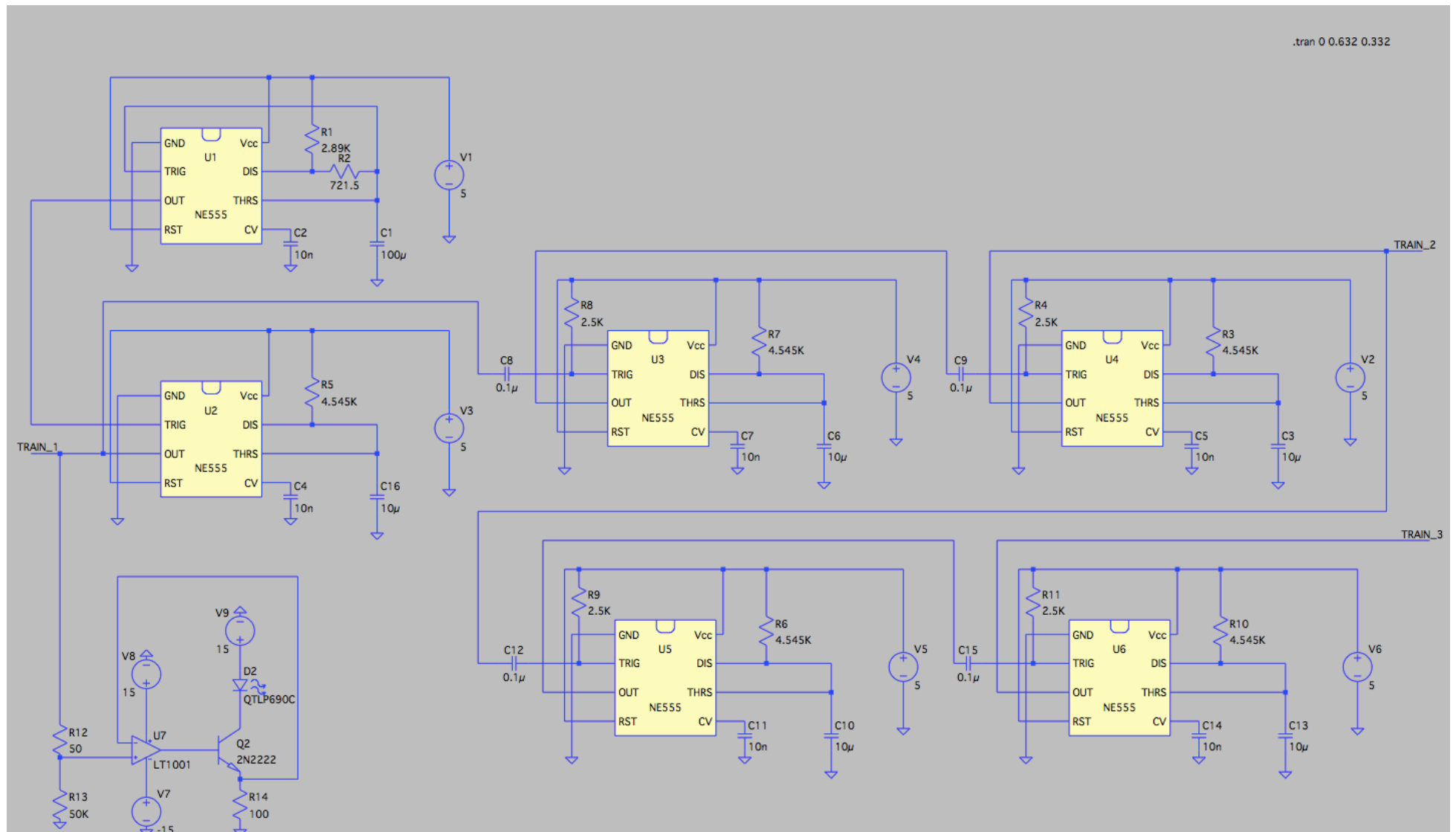

LTSPICE SIMULATION- OUTPUT

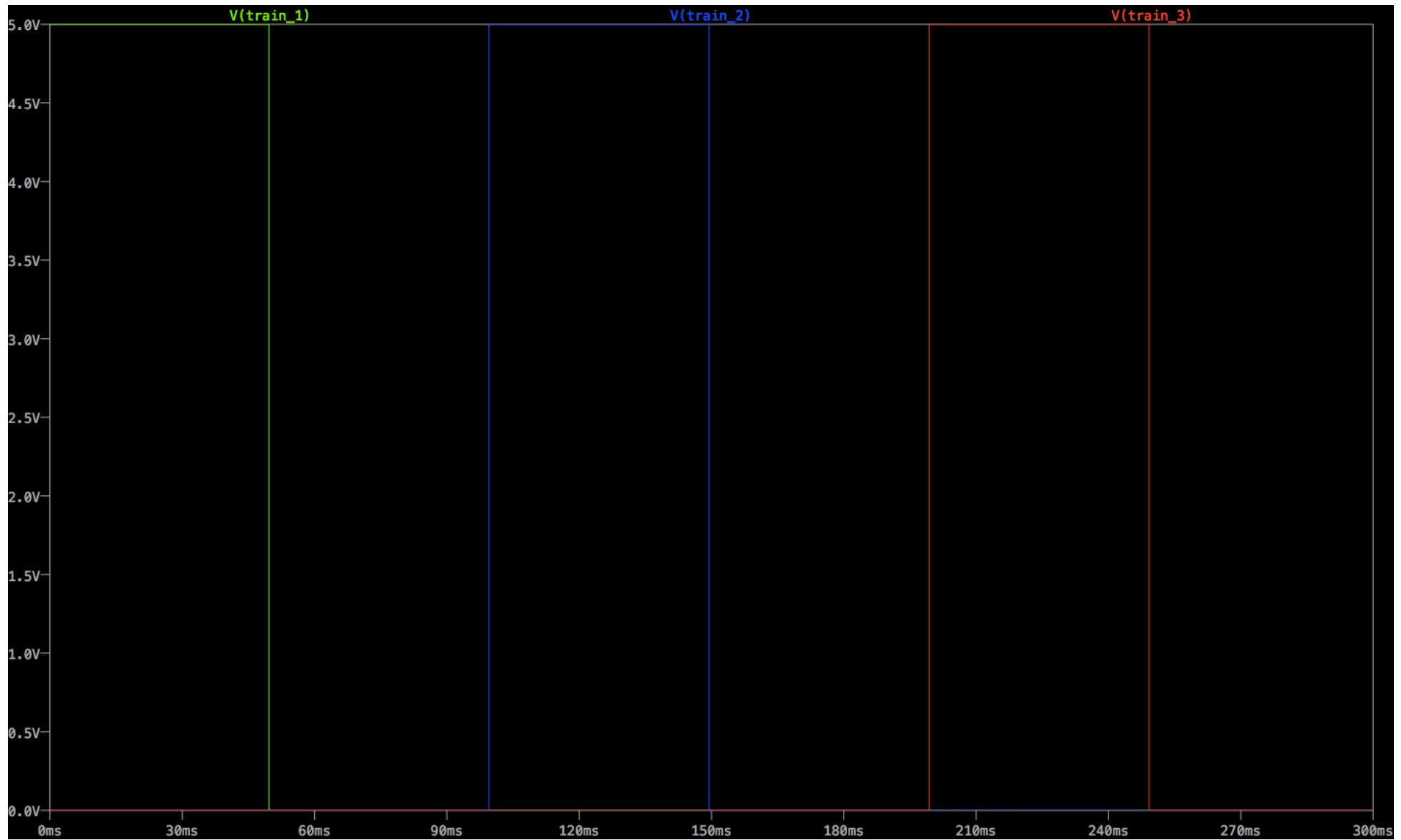

LTSPICE SIMULATION OUTPUT

